Implement the following problem in a MATLAB script m-file.

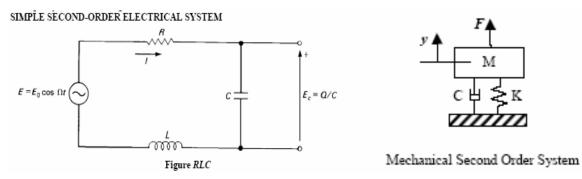


Figure 1: *Left*: Series RCL circuit. *Right*: Mass-spring-damper system. In this problem, at time t = 0, voltage *V* is applied (i.e., a switch is closed), or force *F* is suddenly applied. These input signals are held constant "for all time."

The following discussion is based on *Figure 1*: a series RCL circuit, and a mass-spring-damper system. The two systems are mathematically equivalent to each other. We will assume that the system is *underdamped*... which means when subjected to a constant input, it will oscillate about its final configuration for some time before reaching equilibrium.

The system is initially at "rest" (current is zero; velocity is zero) and there is no energy stored (no current through the inductor and no voltage across the capacitor; no extension in the spring). A step input is suddenly applied at time t = 0 (a switch is closed to apply DC voltage V_s ; a constant force *F* is suddenly applied).

The response of an *underdamped* system to a step input is:

$$x(t) = u_0 \left[1 - e^{-\zeta \omega_n t} (\cos \omega_d t - \gamma \sin \omega_d t) \right]$$

Response:
$$x(t)$$
 (capacitor voltage v_c , displacement $y(t)$)Size of step: u_0 (applied voltage V_s , or static displacement, F/k)Undamped Natural Frequency: $\omega_n = \sqrt{\frac{1}{LC}}$ (electrical), $\omega_n = \sqrt{\frac{k}{m}}$ (mechanical)Damping Ratio: $\zeta = \frac{R}{2}\sqrt{\frac{C}{L}}$ (electrical), $\zeta = \frac{c}{2\sqrt{km}}$ (mechanical)Damped Natural Frequency: $\omega_d = \omega_n \sqrt{1-\zeta^2}$ Normalizing Constant: $\gamma = \frac{\zeta}{1-\zeta^2}$

The equation for x(t) is only valid for *underdamped* system. For an underdamped system: $\zeta < 1$ The function x(t) is a constant (the response's final value), plus an exponentially decaying sinusoid. The system oscillates about it final value; the oscillation eventually dies down. For electrical systems with the components in series (*Figure 1*), u_o is the applied DC voltage V_s , while x(t) is the voltage measured across the capacitor, $v_c(t)$, so:

$$v_c(t) = V_s \left[1 - e^{-\zeta \omega_n t} (\cos \omega_d t - \gamma \sin \omega_d t) \right]$$


The final value of v_c it V_s . In your electrical engineering textbooks, you may have used the *neper frequency*, or *damping factor* $\alpha = \zeta \omega_n$ in the exponential term. A circuit is underdamped when $\alpha < \omega_n$ or $\zeta < 1$.

For **mechanical systems** (*Figure 1*), u_o is the static deflection of the spring, F/k, the applied force divided by the spring constant. x(t) is the spring displacement, y(t), so:


$$y(t) = \frac{F}{k} \Big[1 - e^{-\zeta \omega_n t} (\cos \omega_d t - \gamma \sin \omega_d t) \Big]$$

The final value of y is F/k.

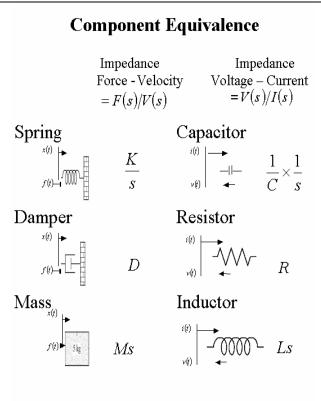Systems that are *overdamped* ($\zeta > 1$ or $\alpha > \omega_n$) or *critically damped* ($\zeta = 1$ or $\alpha = \omega_n$) have different responses, beyond the scope of this exercise.... Perhaps it is for a future assignment.



Source Mise 2004

 

EXERCISE:

Evaluate the system response for:

$\omega_n = 104 \text{ rad/sec}$	$\zeta = 0.3$
$u_0 = 1$ unit (Volts or Force/stiffness)	$0 \le t \le 0.4 (\text{sec})^{\cdot}$

Sample code is given below.

Physical question:

What improvements could be made to the system response? How would you change the parameters?

Programming Question:

Can you develop a code where you interactively input *R*, *C* and *L* (or *c*, *k* and *m*?) Can you use if-ifelse-end statements to create a program that can analyze *underdamped*, *overdamped* and *critically damped* systems for any (practical) combinations of *R*, *C* and *L* (or *D*, *K* and *M*).

```
%Engr 179 Allan Hancock College
%Sherman Wiggin
%Spring 2005
%Response of an underdamped second-order system to a step input
omegan=104 %The natural frequency
zeta = 0.3 %The dampening ratio
u0=1 %Input step size = unity
omegad=omegan*sqrt(1-zeta^2)%The natural damped frequency
gamm_a=zeta/sqrt(1-zeta^2)%non-dimensional parameter (simplifies
notation)
t=linspace(0,0.4) %Creates 100 data points 0 to 0.4
x=u0*(1-exp(-zeta*omegan*t).*(cos(omegad*t)-
gamm_a*sin(omegad*t)))
plot(t,x)
```